 



MOS Transistors as Switches



*n*MOS transistor:

Closed (conducting) when
Gate = 1 (V_{dd}, 5V)

 Open (non-conducting) when
Gate = 0 (ground, 0V)




*p*MOS transistor:

Closed (conducting) when
Gate = 0 (ground, 0V)

Open (non-conducting) when
Gate = 1 (V_{dd}, 5V)

 
For *n*MOS switch, source is typically tied to ground and is used to *pull-down* signals:



when Gate = 1, Out = 0, (0V)

when Gate = 0, Out = Z (high impedance)

 For *p*MOS switch, source is typically tied to V_{dd}, used to *pull* signals *up*:




when Gate = 0, Out = 1 (V_{dd})

when Gate = 1, Out = Z (high impedance)

Note: The MOS transistor is a symmetric device. This means that the drain and source terminals are interchangeable. For a conducting *n*MOS transistor, $V_{DS} > 0V$; for the *p*MOS transistor, $V_{DS} < 0V$ (or $V_{SD} > 0V$).


The CMOS Inverter

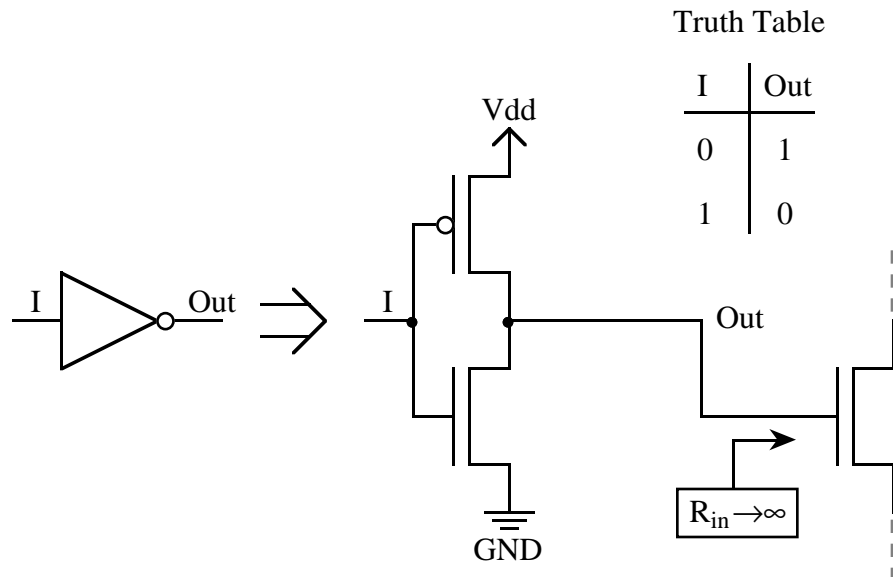

Note: Ideally there is no static power dissipation. When "I" is fully *high* or fully *low*, no current path between V_{dd} and GND exists (the output is usually tied to the gate of another MOS transistor which has a very high input impedance).


Power is dissipated as "I" transitions from 0 \rightarrow 1 and 1 \rightarrow 0 and a momentary current path exists between V_{dd} and GND. Power is also dissipated in the charging and discharging of gate capacitances.

Parallel Connection of Switches

 

$Y = 0$, if A or $B = 1$

 
$$\overbrace{\quad}^{\downarrow} \\ \overbrace{\quad}^{\uparrow} \\ A + B$$



$Y = 1$ if A or $B = 0$


$$\overbrace{\quad}^{\downarrow} \\ \overbrace{\quad}^{\uparrow} \\ \overline{A + B}$$

Series Connection of Switches

 

$Y = 0$, if A and $B = 1$
 
$$\overbrace{\quad}^{\downarrow} \\ \overbrace{\quad}^{\uparrow} \\ A \cdot B$$



$Y = 1$, if A and $B = 0$

$$\overbrace{\quad}^{\downarrow} \\ \overbrace{\quad}^{\uparrow} \\ \overline{A \cdot B}$$

NAND Gate Design


p-type transistor tree will provide "1" values of logic function

n-type transistor tree will provide "0" values of logic function


Truth Table (NAND):

| AB | |
|----|---|
| 00 | 1 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

K-map (NAND):

 


NAND circuit example:

 

$$P_{tree} = \bar{A} + \bar{B}$$

$$N_{tree} = A \cdot B$$

 

NOR Gate Design


p-type transistor tree will provide "1" values of logic function

n-type transistor tree will provide "0" values of logic function


Truth Table:

| AB | |
|----|---|
| 00 | 1 |
| 01 | 0 |
| 10 | 0 |
| 11 | 0 |

K-map:

 


NOR circuit example:

 


$$P_{tree} = \bar{A} \cdot \bar{B}$$

$$N_{tree} = A + B$$

 


What logic gate is this?

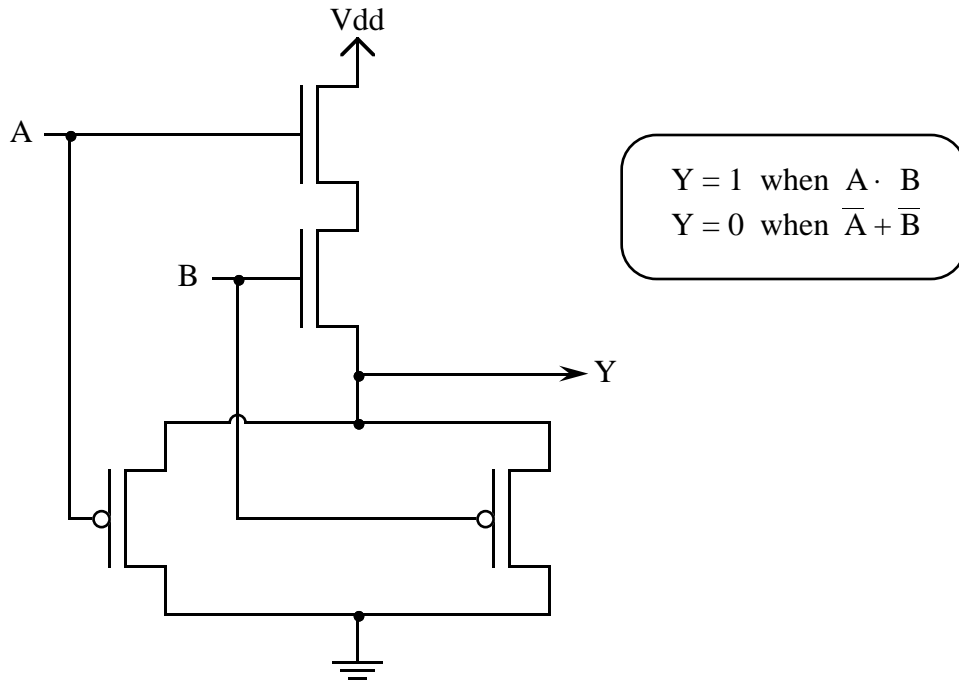


Answer: AND function, but poor design!

 Why? *n*MOS switches cannot pass a logic "1" without a threshold voltage (V_T) drop.



where $V_T = 0.7V$ to $1.0V$ (i.e.,
 threshold voltage will vary)
 output voltage = $4.3V$ to $4.0V$,
 a *weak* "1"

 The n MOS transistor will stop conducting if $V_{GS} < V_T$. Let $V_T = 0.7V$,




As source goes from $0V \rightarrow 5V$, V_{GS} goes from $5V \rightarrow 0V$.

When $V_S > 4.3V$, then $V_{GS} < V_T$, so switch stops conducting.

V_D left at $5V - V_T = 5V - 0.7V = 4.3V$ or $V_{dd} - V_T$.

What about n MOS in series?

 


Only one threshold voltage drop across series of n MOS transistors

For pMOS transistor, V_T is negative.

pMOS transistor will conduct if $|V_{GS}| > |V_{Tp}|$ ($V_{SG} > |V_{Tp}|$),

or $V_{GS} < V_{Tp}$

 

$$V_{Tp} = -0.7V$$


$$V_{GS} = 0V - 5V = -5V$$

conducting

$$V_{GS} < V_{Tp} \text{ or } |V_{GS}| > |V_{Tp}|$$

$$-5V < -0.7V \quad 5V > 0.7V$$

How will pMOS pass a "0"?

 


When $|V_{GS}| < |V_{Tp}|$, stop conducting

So when $|V_{GS}| < |-0.7V|$, V_D will go from 5V → **0.7V**,

a weak "0"

How are both a strong "1" and a strong "0" passed?

 Transmission gate pass transistor configuration




When $I = 1$,

$B = \text{strong } 1$, if $A = 1$;

$B = \text{strong } 0$, if $A = 0$

When $I = 0$, non-conducting

About that AND Gate...

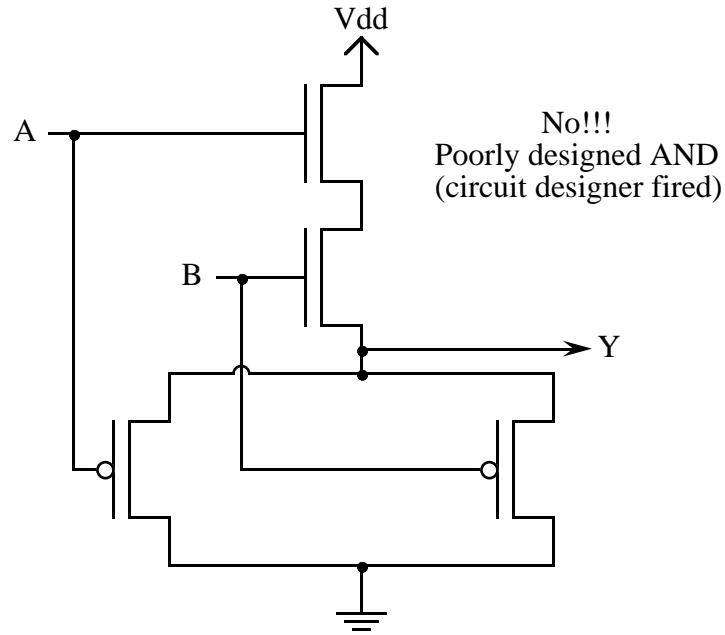

Instead use this,

