 

Lecture 18

SRAM Cell and Column I/O Design


Res Saleh
 Dept. of ECE
 University of British Columbia
 res@ece.ubc.ca

RAS EECE481 Lecture 18 1



SRAM Storage Cell

 Uses six transistors (called 6T memory cell):




Read and write operations use the same port. There is one wordline and two bit lines. The bit lines carry complementary data, a fact that will be used to reduce access time. The cell layout is small since it has a small number of wires (but large relative to DRAM).

RAS

EECE481 Lecture 18

3

CMOS SRAM Cell Design

 


Cell Design

 - Problem: Find w_a , w_d , w_p such that
- 1) minimize cell area
 - 2) obtain good read and write cell margins
 - 3) good soft error immunity
 - 4) good cell read current

in that order

Since the cell is symmetric we need only design three transistor sizes




RAS

EECE481 Lecture 18

4

CMOS SRAM cell design - read

 - Make sure that internal *node a* does not go high enough to turn on M_2
- Use threshold voltage as a maximum allowable voltage at internal node during read; Make current ratio between M_1 and M_3 about 3 to 4
- Want to design device sizes such that read current is high enough to create desired differential voltage on bit lines $\sim 200\text{mV}$ within a specified amount of time




RAS

EECE481 Lecture 18

5

CMOS SRAM cell design - write

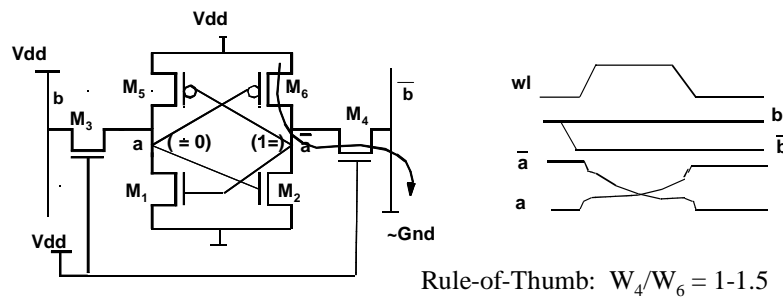- Need to make sure M_4 is strong enough to pull internal node *a* low while M_6 is trying to pull it high
- Use switching threshold as trigger point for regenerative switch point; usually want to make it less than the switching threshold
- This will force inverter M_5 - M_1 switch to new state
- Make ratio of currents between M_4 and M_6 about 3 to 4





RAS

EECE481 Lecture 18

6

SRAM Cell Layout

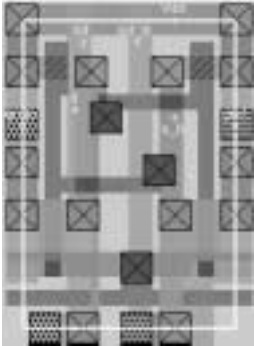

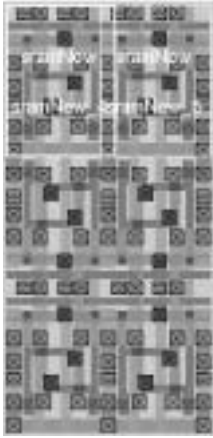

Layout of SRAM cell

- word line running horizontally
- bit lines running vertically
- cross-coupled inverters on top
- access transistors on bottom

Portion of the core array using SRAM cell


- scaled in dimensions compared to single bit cell
- 2 cells across, 3 cells high


replicated in this manner to build the core array

RAS
EECE481 Lecture 18
7

Wordline Capacitance

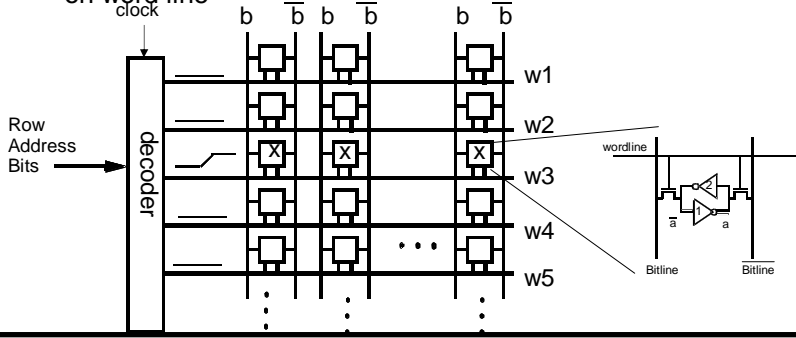- Word line presents a large capacitance to the decoder
- Each cell loads the word line with two transistor capacitances and one wire capacitance (plus wire resistance)
- Total capacitance is the capacitance per cell x number of cells on word line



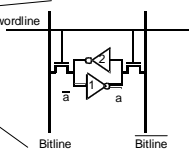

RAS
EECE481 Lecture 18
8

Column I/O Operation

Circuits that perform read and write on the array are column I/O

- Bitline load
 - Can be static or precharged
 - Proper configuration depends on amplifier design
- For read
 - Bit lines must start at around V_{dd}
 - Swings should be small for fast operation
 - Involves Mux and sense amplifier design
- For write
 - Need to drive one of the bitlines to Gnd
 - Mux and write driver design
 - Often use different I/O lines for read and write

RAS


EECE481 Lecture 18

9

Bitline Capacitance

Load capacitance is mostly self-loading of the cells

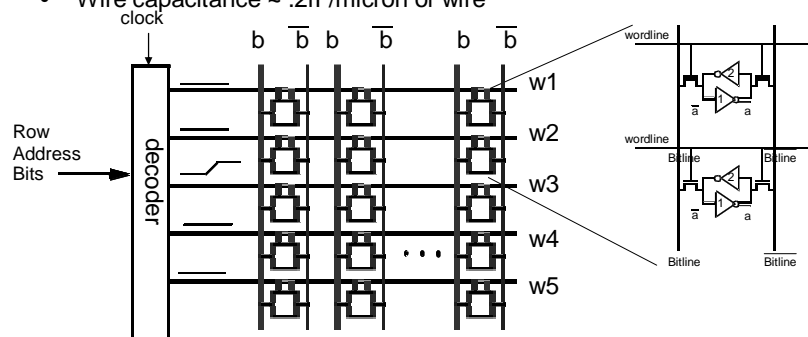- Drain cap and drain contacts (0.5-1 fF) of transistors are shared
 - Junctions are biased at V_{dd} (lower cap than normal)
- Wire capacitance $\sim .2\text{fF}/\text{micron}$ of wire



RAS

EECE481 Lecture 18

10

Read Circuitry

- Precharge bitlines high
- Turn on word line
- One line will slowly discharge
- Wait until bit line reaches required low voltage level
- Turn on column select
- Amplify difference with sense amplifier
- Design sense amplifier based on desired response time and power requirements
- Use precharge based on type of sense amp used.


RAS
EECE481 Lecture 18
13

Column Decoder/Mux

- Need decoder for column address followed by a mux to select column for input or output operations
- Require two outputs to drive complementary pass gates
- Since the requirements for read and write are different can use separate read and write IO lines
- Have PMOS access for the read IO lines, since the read happens near Vdd
- Have NMOS devices for the write IO lines, since you need to drive bitlines to Gnd (see next slide)

RAS
EECE481 Lecture 18
14

Column Muxing – Separate I/O

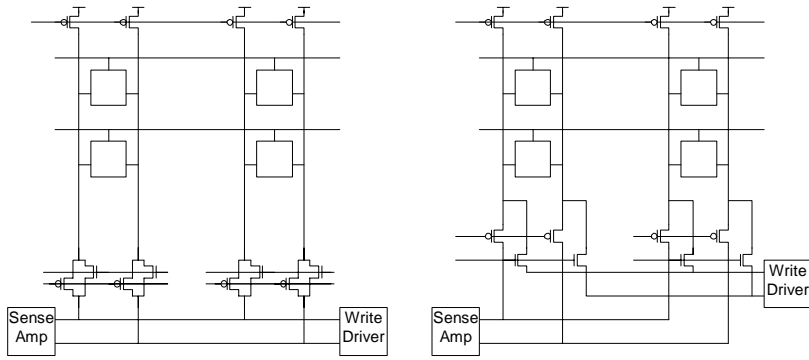


RAS

EECE481 Lecture 18

15

Multi-Level Column Decoding

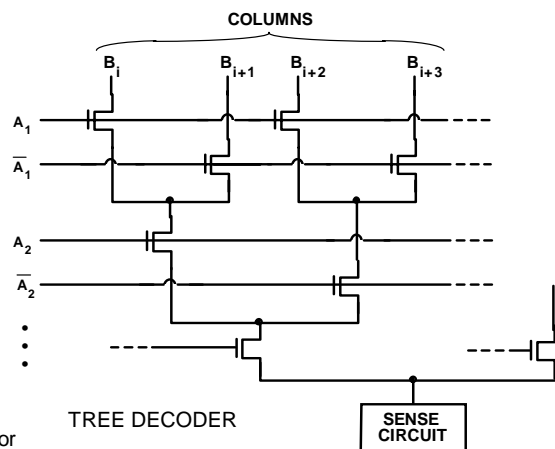- Alternatives for column selection are tree decoder, regular decoder + pass transistor, or some combination of the two
- Shown on the right is a tree decoder
 - switches driven directly by address bits and their complements
 - total of 2^{M+1} devices
 - large devices to reduce resistance
 - long paths -> large C -> SLOW
- To speed up, add buffers or use adjust sizing of devices




RAS

EECE481 Lecture 18

16

Other Options for Column Decoder/Mux

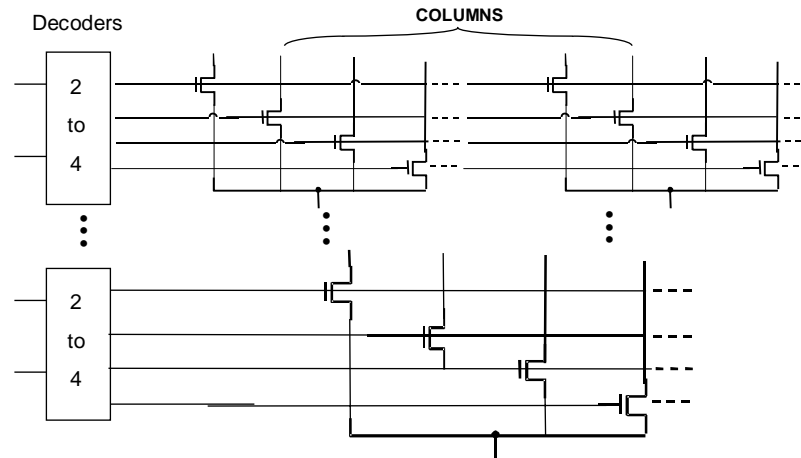

RAS

EECE481 Lecture 18

17

Building Amplifiers

- We need an amplifier to handle small voltage swings on the bit lines for fast operation
- Normally you need to choose between
 - Drawing DC power (diff. sense amplifier)
 - Using a clock edge (latch-based amplifier)
(to turn DC power on only when the signal is present)
- For CMOS logic gates
 - When input is at VDD or Gnd, one of the transistors is off
 - Nothing can happen until this transistor turns on
 - And even then you need to wait some more for gate to switch
 - Sitting in low gain region of transfer curve
- For an amplifier
 - Want to be in high-gain region (saturation)


RAS

EECE481 Lecture 18

18

Latch-based Sense Amplifier

 - It must sense a very small signal
- It must consume a small area
 - Need one for each bitline
 - Or sets of bitline (4 or 8)
- Simplest design:
 - Two back-to-back inverters
 - Add a clocked pulldown
- Once Bit and Bit_b are established, turn on pulldown device to activate inverters
- Side with lower voltage will drop to 0V while the other side stays high




RAS

EECE481 Lecture 18

19

Using Clocks and Regeneration

 - Three stages of operation
 - Precharge
 - Sample
 - Regenerate
- At the end of sample
 - Small bitline voltage on sense and sense_b
- Regenerate
 - M2 and M3 turn on
 - Voltage difference causes current difference
 - Which causes larger voltage difference



RAS

EECE481 Lecture 18

20